

Keywords: DS1864, current DAC, voltage DAC, current to voltage

APPLICATION NOTE 4075

How to Use the DS1864's Current DACs as Voltage DACs

Jul 20, 2007

Abstract: This article describes how to convert the current DACs in the DS1864 SFP laser controller/monitor to a voltage output by using standard components.

The Current DACs

The **DS1864** contains two 8-bit current-sink DACs with 1.5mA or 0.5mA selectable full-scale range. The DAC outputs must be at a voltage level between 0.7V and the DS1864's V_{CC}.

Current-to-Voltage Conversion

An operational amplifier in differential amplifier configuration is used to convert the 0.5mA full-scale current-mode output to 1V full-scale voltage-mode output (**Figure 1**).

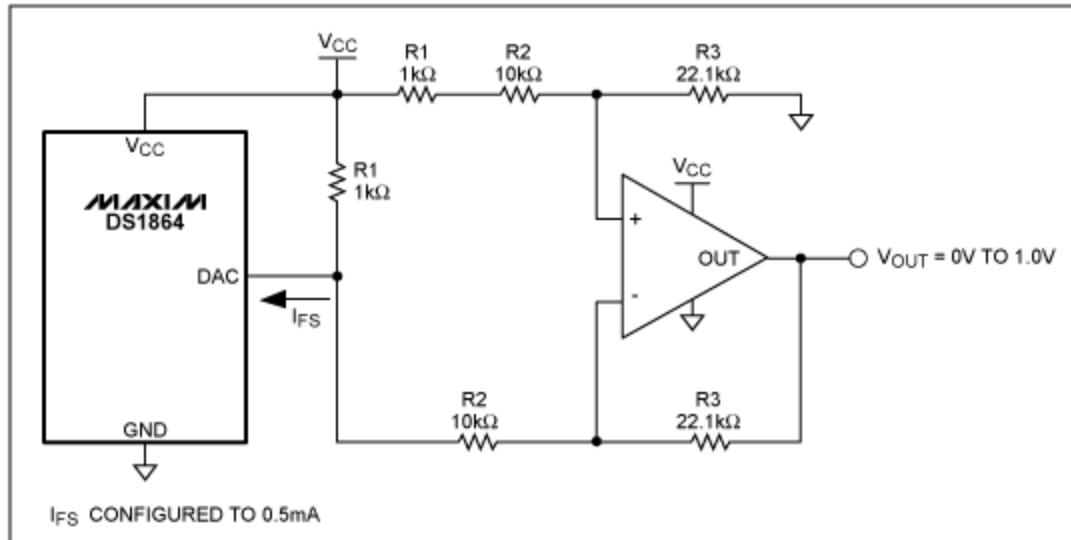


Figure 1. Circuit shows current-to-voltage conversion.

Compact Solution

Using a chip-scale packaged op amp and 0201 resistors will provide the most compact solution. The **MAX4233** is a two-channel op amp available in 1.5mm x 2mm 10-bump UCSP™.

Output Voltage Calculation

The output voltage is calculated in Equation 1.

$$V_{OUT} = \frac{(I_{DAC} \times R1) \times R3}{R1 + R2} \quad (\text{Eq. 1})$$

Using the values shown in the Figure 1 drawing, the maximum output voltage is 1.005V when the DAC current is 0.5mA. To minimize offset and gain errors, 1% tolerance resistors should be used. Further, R1 should be selected so that the voltage at the DAC pin never falls below 0.7V.

UCSP is a trademark of Maxim Integrated Products, Inc.

Related Parts

DS1864	SFP Laser Controller and Diagnostic IC	Free Samples
MAX4233	High-Output-Drive, 10MHz, 10V/μs, Rail-to-Rail I/O Op Amps with Shutdown in SC70	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 4075: <http://www.maximintegrated.com/an4075>

APPLICATION NOTE 4075, AN4075, AN 4075, APP4075, Appnote4075, Appnote 4075

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>