

TI Audio's New High Efficiency AD Modulation Scheme for Class-D Amplifiers

Avi Yashar, Audio Amplifier Products



Battery-operated portable Bluetooth and Wi-Fi speakers have grown in popularity around the world. Designers are often cost and space-restricted for battery capacity. Hence, an efficient amplifier is paramount to maximizing battery life. To further improve efficiency in Class-D amplifiers, TI developed a proprietary modulation scheme first implemented in the high-power TPA3221 Class-D amplifier, called High Efficiency AD modulation (HEAD). HEAD modulation differentiates itself with benefits such as reduced idle power losses, improved EMI performance, and even less pop noise than AD modulation. This makes TPA3221 an ideal choice for wireless speakers and other applications where efficiency, system size and cost are critical. This Tech Note elaborates on how HEAD Modulation produces differential output for a bridge-tied-load (BTL) system shown in Figure 1, and the mechanisms behind the benefits mentioned above.

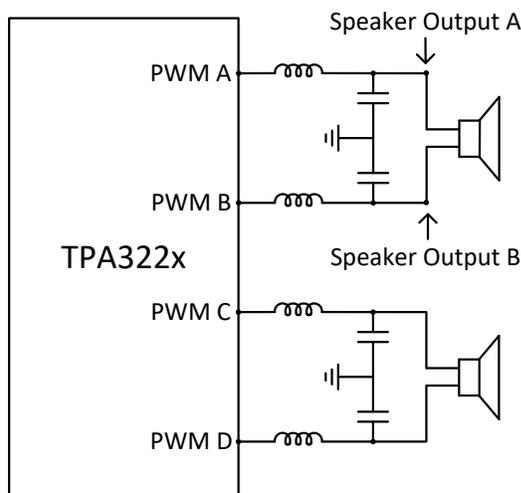


Figure 1. BTL Output Configuration

In BTL, the audio signals leave the amplifier as a pair of PWM signals (PWM A and B). They then filter through LC networks, becoming analog signals (Speaker Output A and B). These outputs result in a differential signal across the speaker. To understand the TPA3221's high efficiency modulation scheme, let's start with the idle state (no audio signal). Figure 2 shows different levels of an audio signal. Figure 3 and Figure 4 show AD and HEAD modulation across the signal chain with different level audio signals. The figures are color coordinated, red representing the idle state.

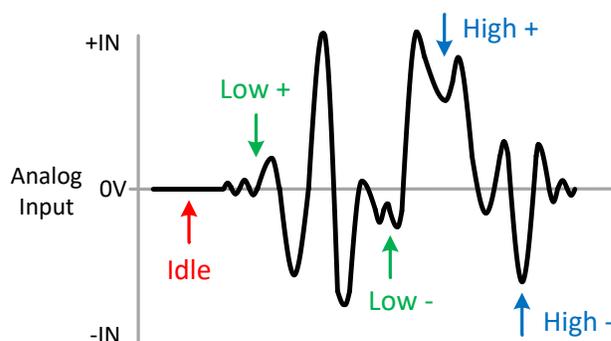


Figure 2. Analog Audio Signal

AD Modulation achieves idle (0V seen by speaker) with 50% duty cycle at PWM A and B, resulting in $+1/2$ PVDD at Speaker Output A and $+1/2$ PVDD at Speaker Output B after the LC filter. The speaker sees the voltage at A minus the voltage at B and therefore, experiences zero volts. HEAD differs by using two lower duty cycle signals for idle instead of 50%. This results in a less-than-half-PVDD at Speaker Output A and Speaker Output B, but since they are still equal, the differential across the speaker is also zero volts.

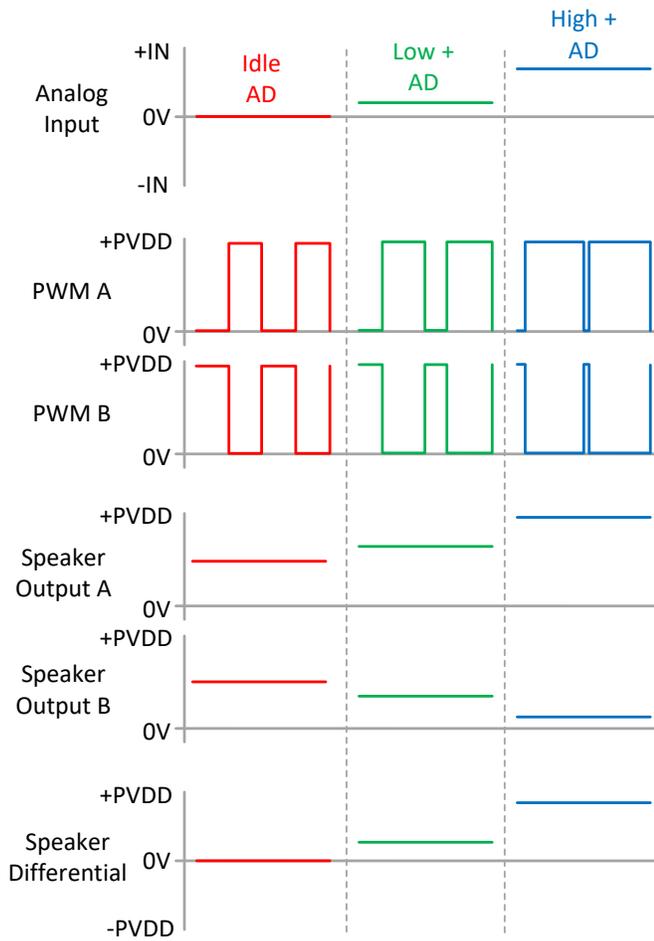


Figure 3. AD Modulation

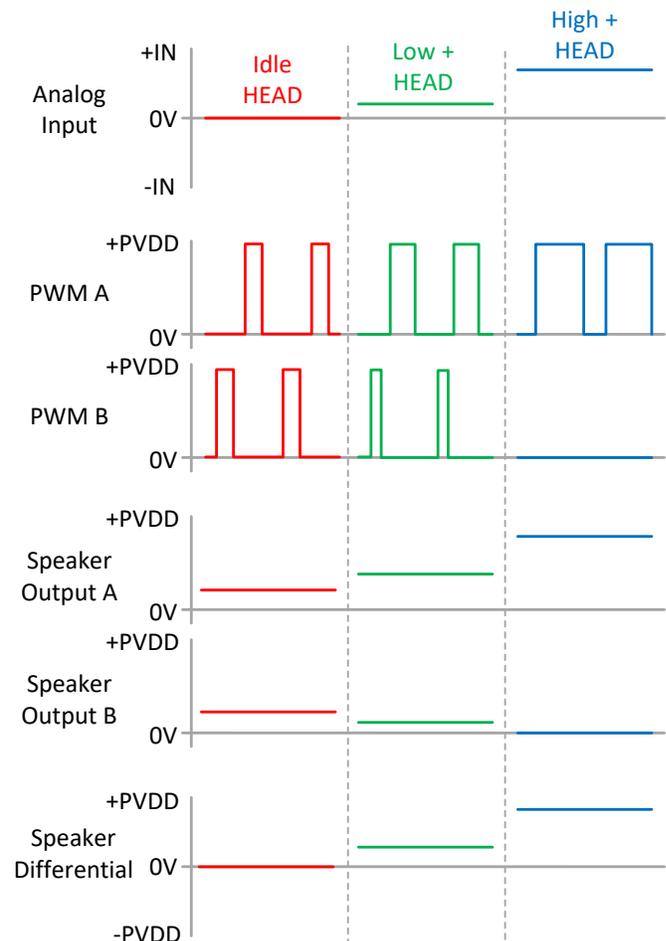


Figure 4. HEAD Modulation

In AD and HEAD modulation, a low-magnitude differential output is generated by increasing the duty cycle of one PWM signal and decreasing the other one relative to idle. In Figure 3 and Figure 4, the duty cycle of PWM A is increased and PWM B is decreased to create a positive differential. For AD, PWM A and B always change at a rate equal in magnitude and opposite in direction, from idle all the way to max output. In HEAD, since the idle state is defined at a lower duty cycle than 50%, as PWM A increases PWM B reaches 0% duty cycle before the max differential output is achieved across the speaker. Above this threshold in HEAD, PWM A increases its duty cycle at twice the prior rate, since PWM B cannot decrease further than zero to contribute to the differential output.

TI engineers carefully optimized the duty cycle for the HEAD modulation idle state. An adequately low duty cycle for the idle state results in lower idle power losses and improved EMI performance. Too low of a duty cycle would result in poor performance and a loss of these benefits.

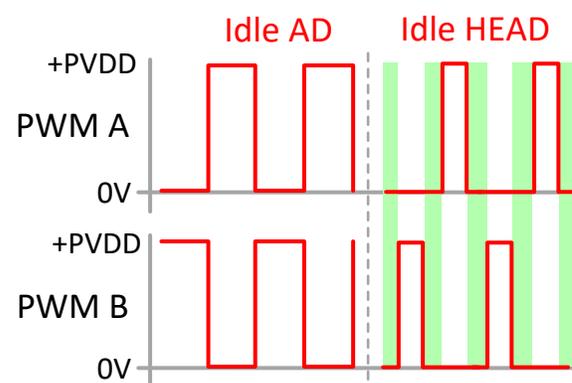


Figure 5. AD and HEAD Idle PWM

Visualized in Figure 5, the HEAD idle state has periods where both PWM A and PWM B are at 0V. The lower duty cycle reduces the RMS current, as the peak-to-peak current is proportional to the duty cycle. Consequently, both conduction losses due to ripple current through RDSON and switching losses are reduced. Figure 6 shows the improvement of HEAD idle current compared to AD idle current for the TPA3221 amplifier in BTL.

The narrower pulses also benefit EMI performance due to their reduced spectral content, emitting a significantly lower magnitude of high frequency energy. Lastly, since the idle duty cycle is lower in HEAD than AD, the pop sound generated by ramping up to and down from idle in HEAD is a small fraction of that in AD.

The improvements of HEAD make it a highly desirable modulation scheme for battery-powered speakers and other applications concerned with efficiency, EMI, or pop noise. As the world continues to demand louder, better-sounding, high-resolution Bluetooth and wireless speakers with longer battery life, TI Audio provides innovative solutions to take your products to the next level.

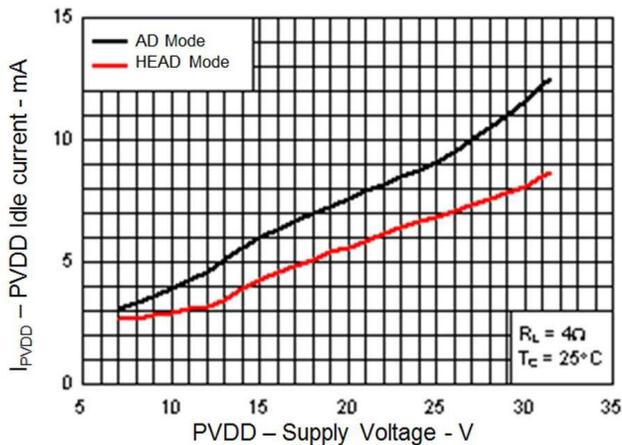


Figure 6. HEAD and AD Idle Current in BTL

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated